

Ross Distortion

This layout will allow you to build a Ross Distortion clone. Tantalum caps are noted but can be replaced with electrolytics of the same value. Note polarity of these caps. This unit over the years has had various dual op-amps, and the Texas Instruments RC4558 was in the unit I used for reference. TL072 and other duals will work. Diodes are germanium 1N270, but I do believe 1N34a will also work.

